

Q: A digital computer has a common bus system for 8 registers of 16 bits each. The bus is constructed with multiplexers. How many multiplexers in the bus and What size of multiplexers are needed?

A: There are 16 multiplexers, The size of multiplexers 8 X 1.